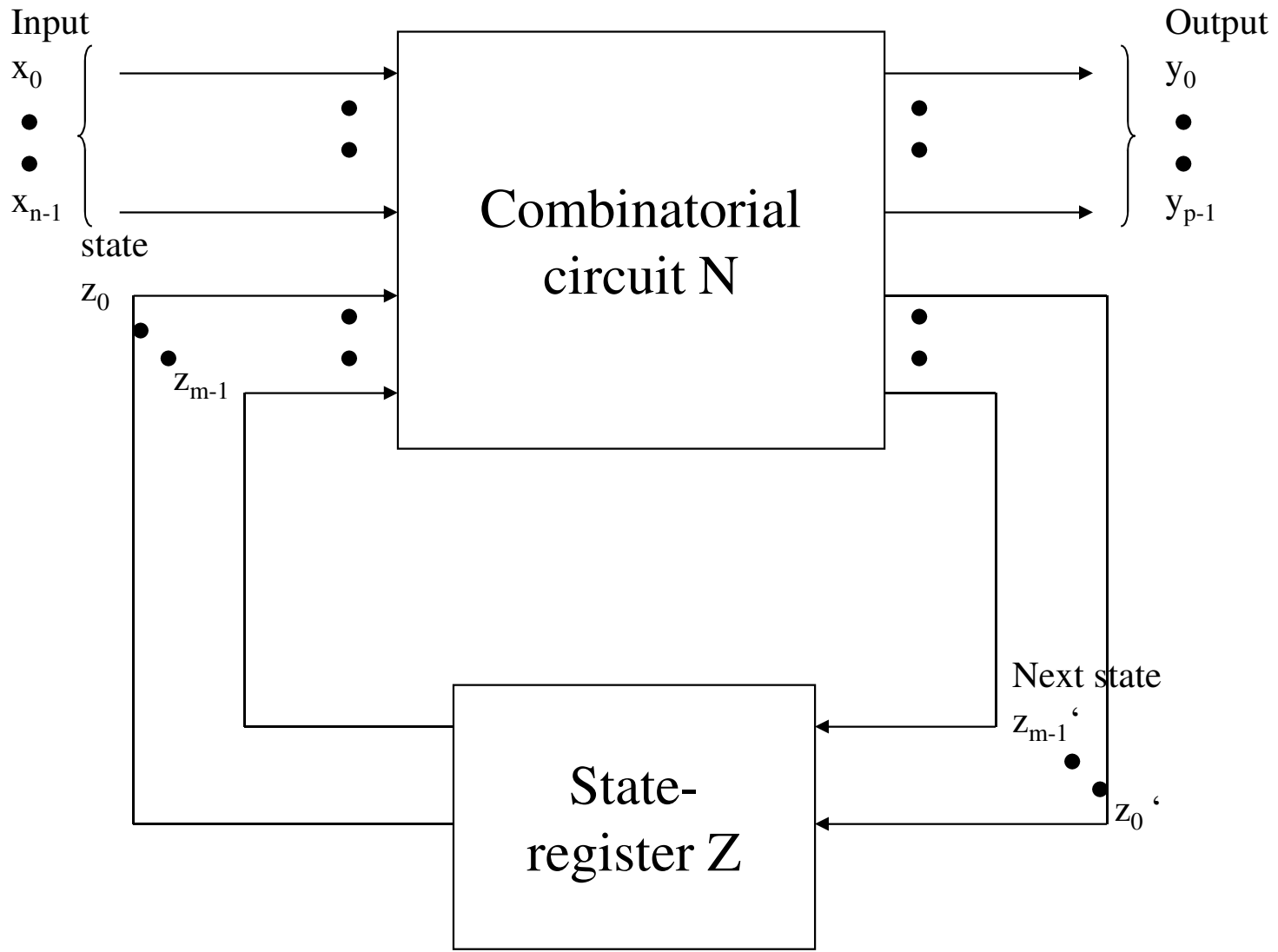


Definition:

A sequential circuit is a circuit whose output depends on the actual input and the actual inner state.




Definition:


An element to store the values 0 and 1 is called a **flipflop**.

A flipflop can change between its states according to an appropriate input combination.

Definition:

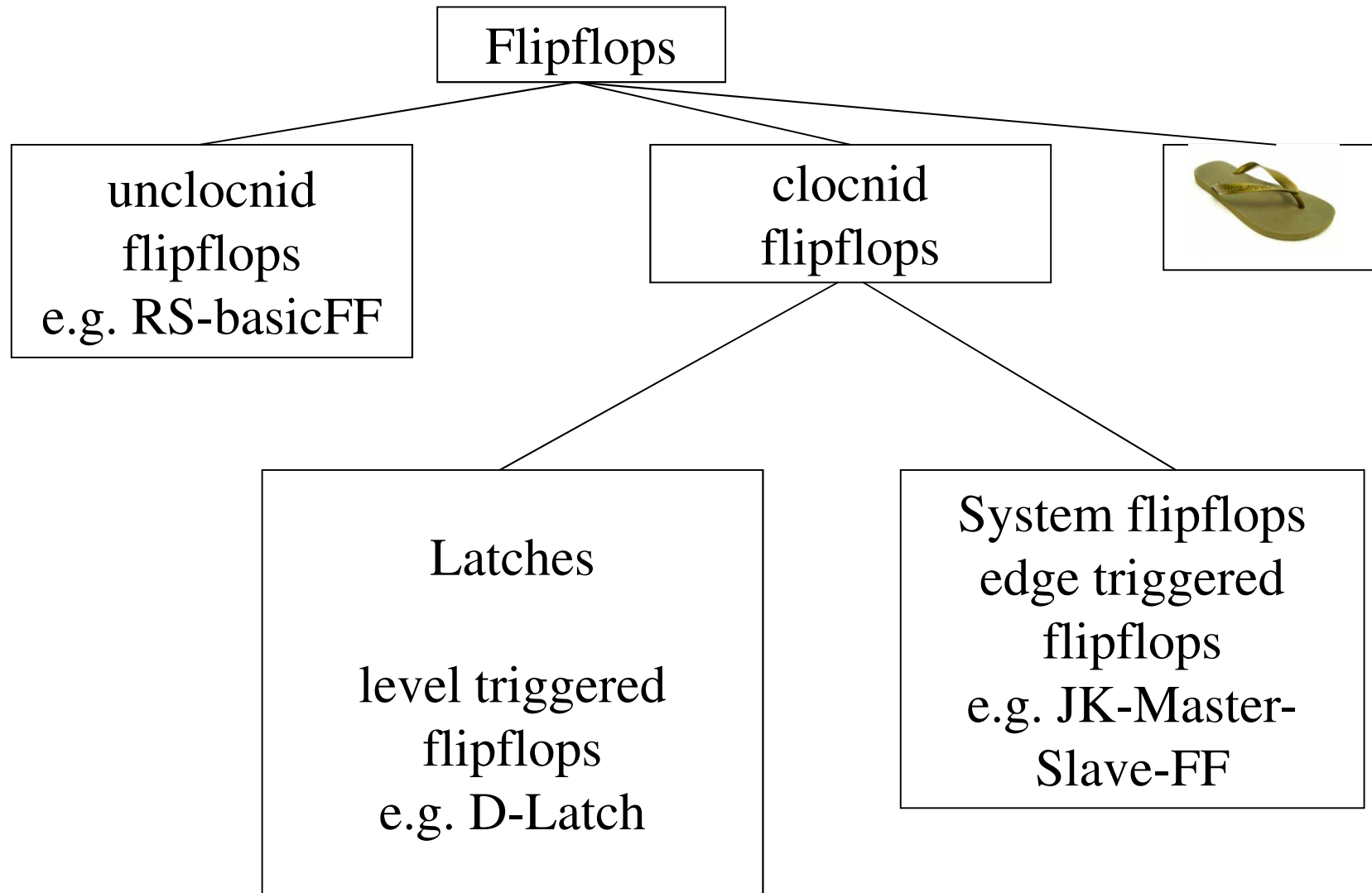The state Z of a sequential circuit is an m -tuple $(z_{m-1}, z_{m-2}, \dots, z_1, z_0)$ with components $z_i \in B = \{0, 1\}$. Each component z_i stands for a flipflop.



 

x	z_1	z_0	z_1'	z_0'	y
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	X	X	X
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	X	X	X


KV-diagrams:

$$z_0' = x \bar{z}_0 \bar{z}_1$$


$$z_1' = x z_0 + x z_1$$

$$y = x z_1$$


The complete sequential circuit:

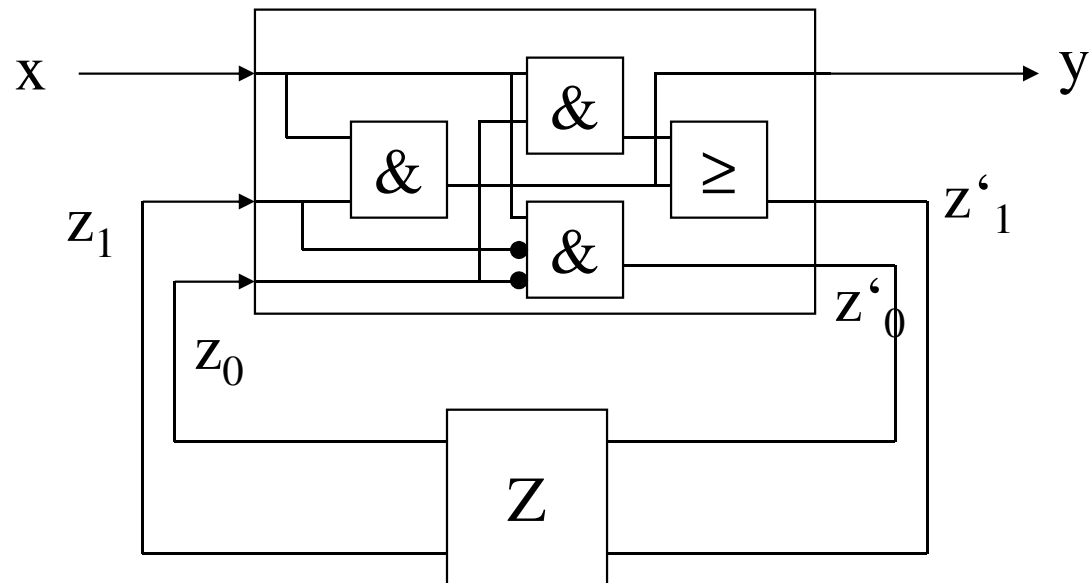


Das r-s-Flipflop

 

r	s	Q	Q^*
0	0	Q_{alt}	Q^*_{alt}
0	1	1	0
1	0	0	1
1	1	0	0

 


 


\bar{r}	\bar{s}	Q	Q^*
1	1	Q_{alt}	Q^*_{alt}
1	0	1	0
0	1	0	1
0	0	1	1

Truth table:

clk	r	s	Q	Q*
0	0	0	Q_{alt}	Q^*_{alt}
0	0	1	Q_{alt}	Q^*_{alt}
0	1	0	Q_{alt}	Q^*_{alt}
0	1	1	Q_{alt}	Q^*_{alt}
1	0	0	1	0
1	0	1	1	0
1	1	0	0	1
1	1	1	forbidden	

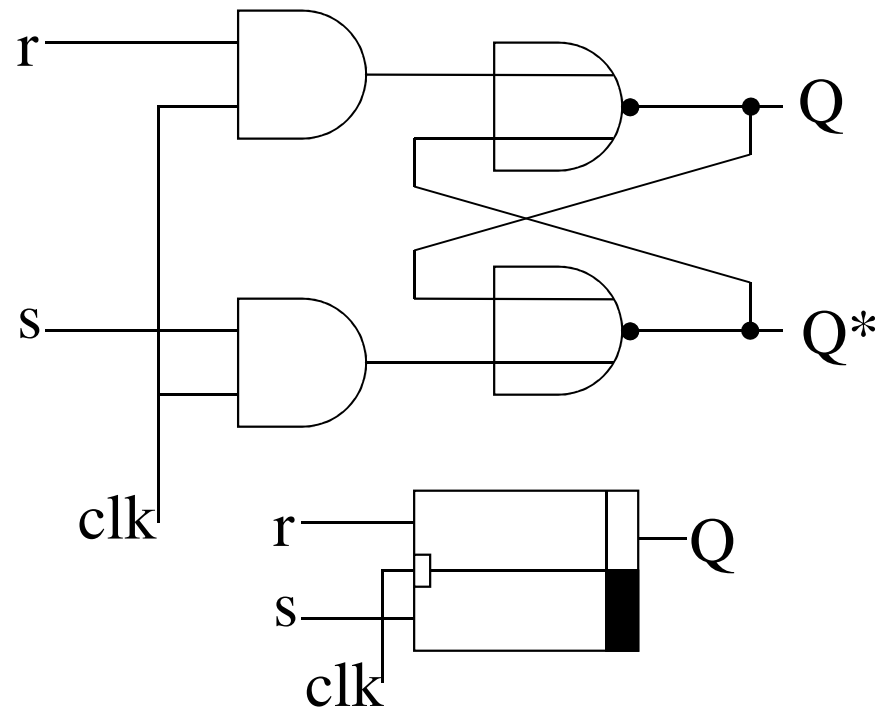


Nand Logic

 

D-Latch


Truth table:

clk	D	Q	Q*
0	0	Q_{alt}	Q^*_{alt}
0	1	Q_{alt}	Q^*_{alt}
1	0	0	1
1	1	1	0

 


Saving one inverter

clk	D	Q	Q*
0	0	Q_{alt}	Q^*_{alt}
0	1	Q_{alt}	Q^*_{alt}
1	0	0	1
1	1	1	0


 


Negativ level triggered flipflop


clk	D	Q	Q*
0	0	0	1
0	1	1	0
1	0	Q_{alt}	Q^*_{alt}
1	1	Q_{alt}	Q^*_{alt}

 


Master-Slave D-Flipflop

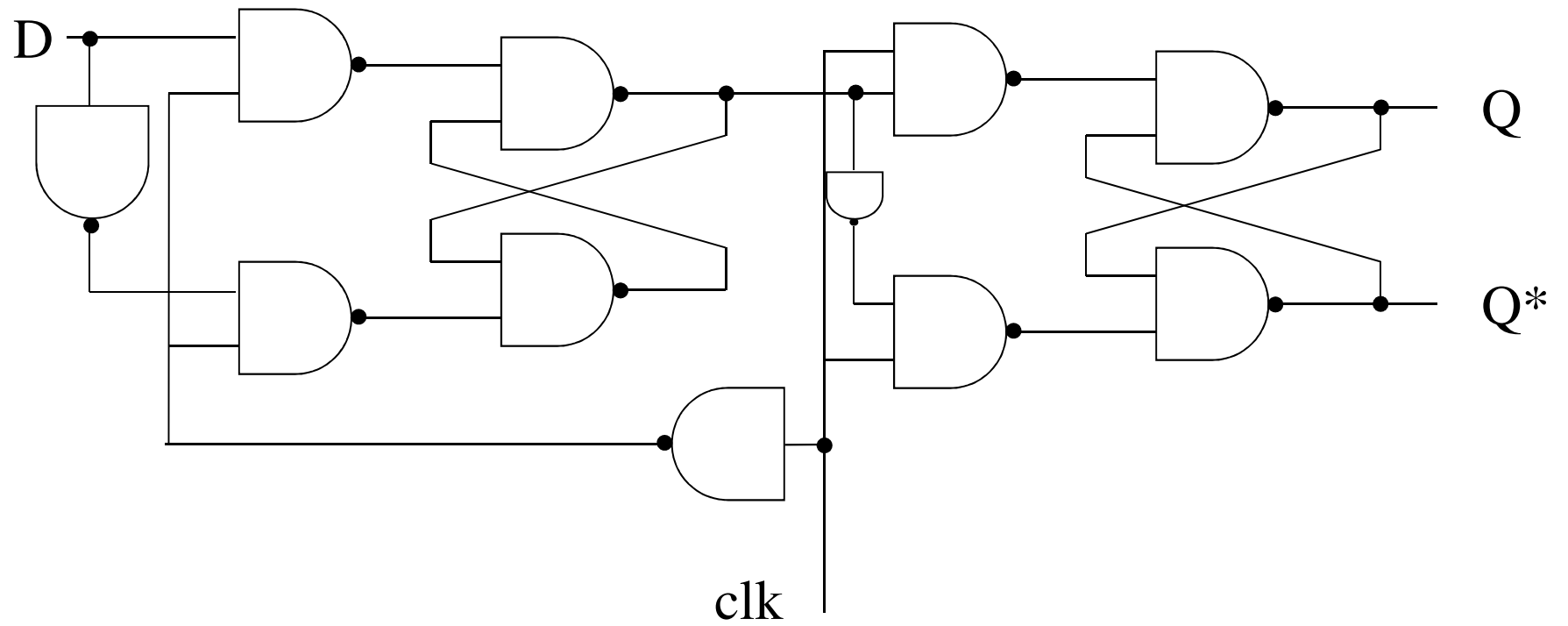 



Master-Slave D-Flipflop, Timing

 

 - t_1 : Master stores
- t_2 : Slave opens
- t_3 : Slave stores
- t_4 : Master opens




 


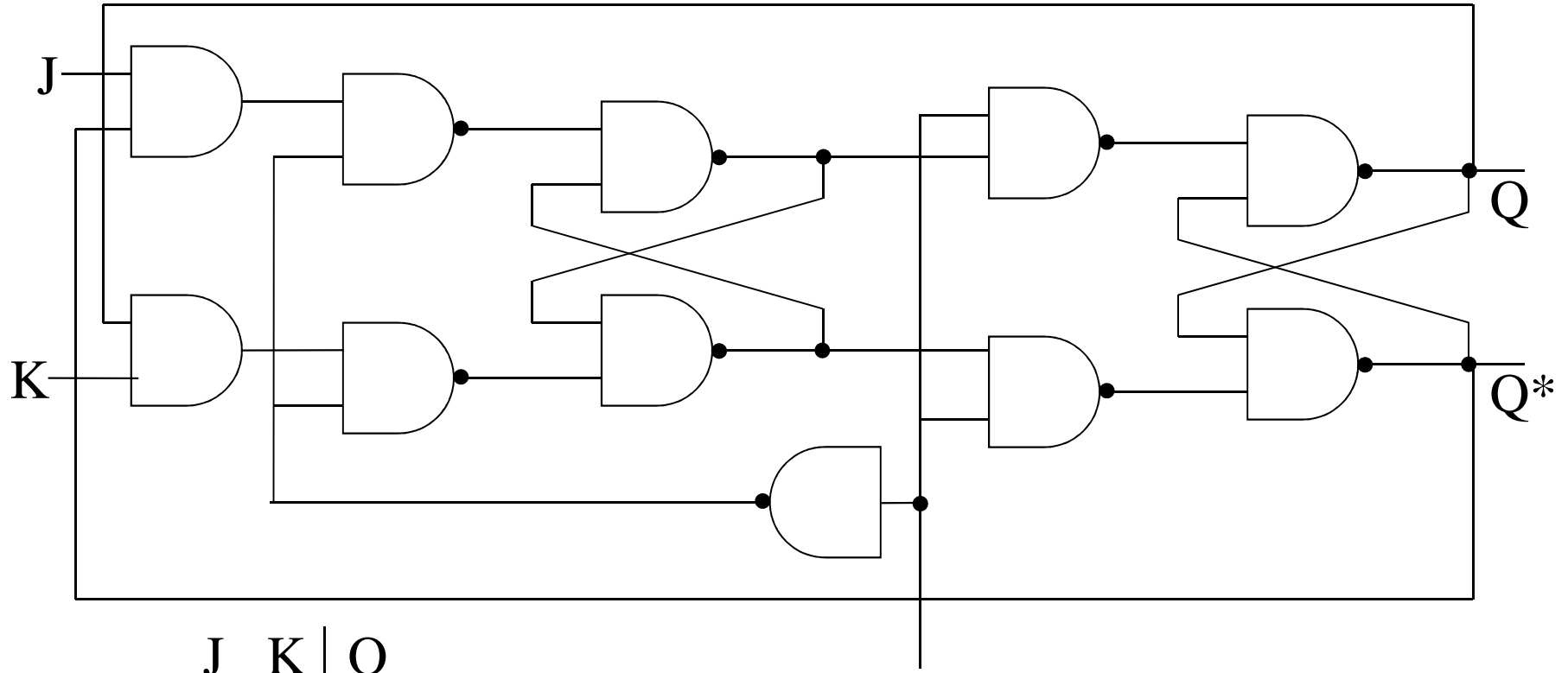





J	K	Q
0	0	Q_{alt}
0	1	0
1	0	1
1	1	$\overline{Q_{alt}}$

clk



  

T	Q
0	Q_{alt}
1	$\overline{Q_{alt}}$

    

Positive
level triggered


Negative
level triggered

Positive
edge triggered

Negative
edge triggered

D

Clk

 

Example:


FSM for detecting even parity for bit serial binary value

$$A = (X, Y, Z, \delta, \lambda) \quad X = \{ 0,1 \}$$

$$Y = \{ 0,1 \}$$

$$Z = \{ 0,1 \}$$

δ	0	1
0	0	1
1	1	0

 

λ	0	1
0	0	1
1	1	0

x	z	z'	y
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

Example:
Coke-Automaton

$$A = (X, Y, Z, \delta, \lambda)$$

$$X = \{ 0.50, 1.-, \text{ni}, \text{back} \}$$

$$Y = \{ \text{Cola}, 0.50, 1.-, \text{no} \}$$

$$Z = \{ \text{Empty}, 0.50, 1.- \}$$

δ	0.50	1.-	ni	back
empty	0.50	1.-	empty	empty
0.50	1.-	empty	0.50	empty
1.-	empty	0.50	1.-	empty

λ	0.50	1.-	ni	back
empty	no	no	no	no
0.50	no	Cola	no	0.50
1.-	Cola	Cola	no	1.-

Wertetabelle:

x_1	x_0	z_1	z_0	z_1'	z_0'	y_1	y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0
0	0	1	0	1	0	0	0
0	0	1	1	X	X	X	X
0	1	0	0	0	1	0	0
0	1	0	1	1	0	0	0
0	1	1	0	0	0	1	1
0	1	1	1	X	X	X	X
1	0	0	0	1	0	0	0
1	0	0	1	0	0	1	1
1	0	1	0	0	1	1	1
1	0	1	1	X	X	X	X
1	1	0	0	0	0	0	0
1	1	0	1	0	0	0	1
1	1	1	0	0	0	1	0
1	1	1	1	X	X	X	X

KV-Diagrams:

z_1'

	x_0		
			1
x_1		d	d
	1	d	d
			1

z_0

z_1

y_1

	x_0		
		1	1
x_1		d	d
		d	d
			1

z_0

z_1

$$z_1' = \overline{x_0} \overline{x_1} \overline{z_0} z_1 + \overline{x_0} \overline{x_1} z_1 + x_0 \overline{x_1} \overline{z_0}$$

$$z_0' = \overline{x_0} \overline{x_1} z_1 + \overline{x_0} \overline{x_1} \overline{z_0} + x_0 \overline{x_1} \overline{z_0} z_1$$

z_0'

	x_0		
			1
x_1		d	d
		d	d
	1		

z_0

z_1

y_0

	x_0		
			1
x_1		d	d
	1	d	d
			1

z_0

z_1

$$y_1 = x_1 z_1 + x_0 z_1 + \overline{x_0} \overline{x_1} \overline{z_0}$$

$$y_0 = x_1 z_0 + \overline{x_0} \overline{x_1} z_1 + x_0 \overline{x_1} z_1$$

Implementation as an FPLA:

